

# Unit 1

# Basic Digital Logic

---

EL-GY 9463: INTRODUCTION TO HARDWARE DESIGN

PROFS. SUNDEEP RANGAN, SIDDHARTH GARG


# Learning Objectives

---

- ☐ Write **SystemVerilog** descriptions for simple hardware **modules**
- ☐ Draw high-level **block diagram** representations of the module implementations
- ☐ Identify the **critical path** and its delay from the block diagram
- ☐ Implement simple functions in synchronous logic
- ☐ Visualize signals in a **timing diagram**
- ☐ Write a **testbench** for the hardware modules
- ☐ **Simulate**, and **synthesize** the SystemVerilog using **Vivado** tools
- ☐ Extract **value-change dump** (VCD) files and **synthesis reports** and process them in python

# Outline

---

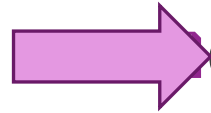

## Combinational Logic

- ☐ Timing Diagrams for Combinational Logic
- ☐ Registers, Clocks and Sequential Logic
- ☐ Simulating and Synthesizing Simple Modules in Vivado




# Simple Example: ReLU + Linear

**Goal:** Implement a module for the function

$$y = \max\{ax + b, 0\}$$

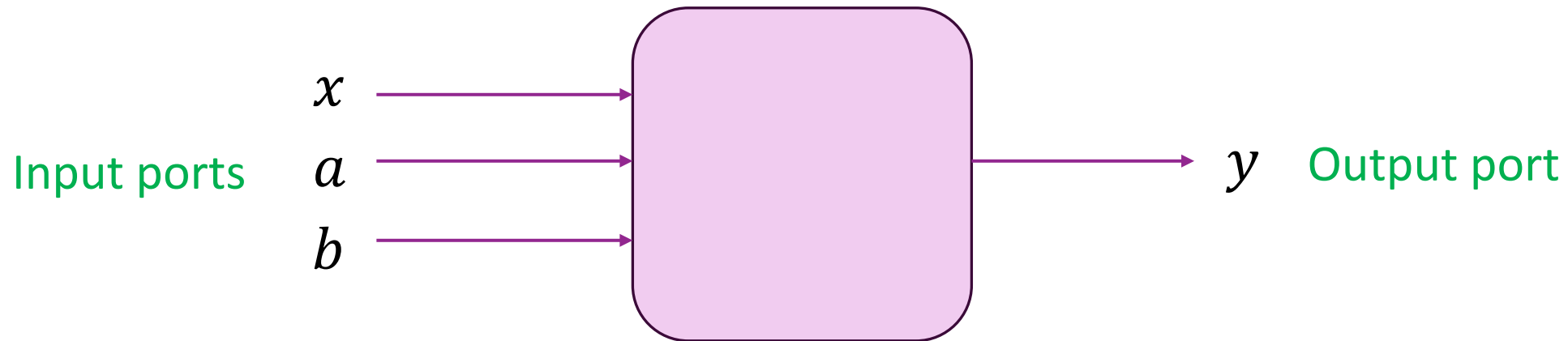- Linear function + ReLU
- Used widely in machine learning



# SystemVerilog Description

## ❑ SystemVerilog:

- Language for **behavioral** description
- What the module should do

## ❑ Each block is a **module**

- Has inputs and outputs
- Logical mapping from inputs to outputs

## ❑ Description is behavioral only

- Does not say how it will be implemented
- We discuss that later

```
module relu_lin (  
    input logic int x,  
    input logic int a,  
    input logic int b,  
    output logic int y  
);  
    always_comb begin  
        logic int mult_out, add_out;  
        mult_out = x * a;  
        add_out = mult_out + b;  
        y = (add_out > 0) ? add_out : 0;  
    end  
endmodule
```

# Module Components in SV

```
module relu_lin (  
    input logic int x,  
    input logic int a,  
    input logic int b,  
    output logic int y  
);  
    always_comb begin  
        logic int mult_out, add_out;  
        mult_out = x * a;  
        add_out = mult_out + b;  
        y = (add_out > 0) ? add_out : 0;  
    end  
endmodule
```

❑ Module name

❑ Ports:

- Defines inputs and outputs
- Each has a type (e.g., int)

❑ Behavioral description

- In this case, a **combinational block**
- Sequence of operations
- From input to output

# System Verilog vs Verilog

---

## ❑ Verilog

- Created in 1983-84
- Standardized in 1995. Became mainstream RTL
- Largely used for legacy designs

VERILOG

## ❑ System Verilog (this unit)

- Developed in 2002
- Extends Verilog
- Better abstraction, parameterization
- Significantly improved testbench
- Overwhelming design choice today

SystemVerilog

# Synthesis


## Behavioral Description

*What module does?*

Ex: Verilog, HLS, SV


```
module relu_lin (  
    input logic int x,  
    input logic int a,  
    input logic int b,  
    output logic int y  
);  
    always_comb begin  
        logic int mult_out, add_out;  
        mult_out = x * a;  
        add_out = mult_out + b;  
        y = (add_out > 0) ? add_out : 0;  
    end  
endmodule
```

## Synthesis

 

## Implementation

*How functions maps to hardware*

 



# Implementation Depends on the Target

❑ Components for implementation depend on target

❑ Gate-level netlist (classic implementation)


- AND, OR, XOR, NOT gates
- Multiplexers, adders, subtractors, flip-flops, latches

❑ Technology-mapped **standard cells** for ASICs

- NAND2\_X1, DFFR\_X2, AOI21\_X4, INV\_X1
- Actual cells in foundry's library

❑ FPGA primitives

- DSP units, LUTs, BRAM, ...

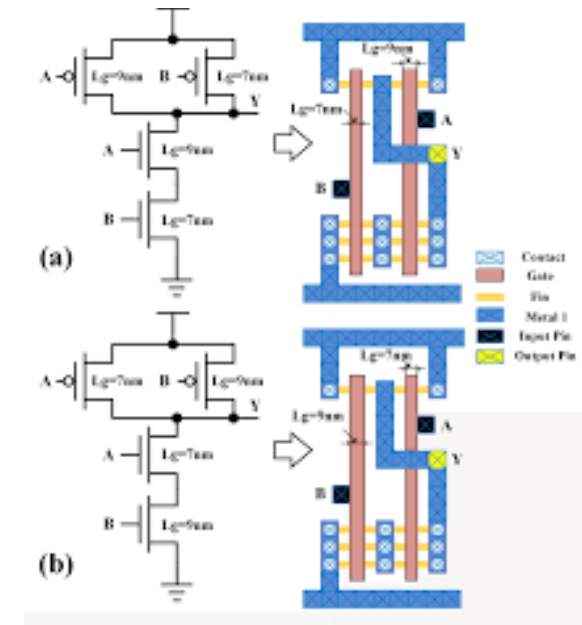


FinFET NAND gate

Cui, Tiansong, et al. "An exploration of applying gate-length-biasing techniques to deeply-scaled FinFETs operating in multiple voltage regimes." *IEEE Transactions on Emerging Topics in Computing* 6.2 (2016): 172-183.
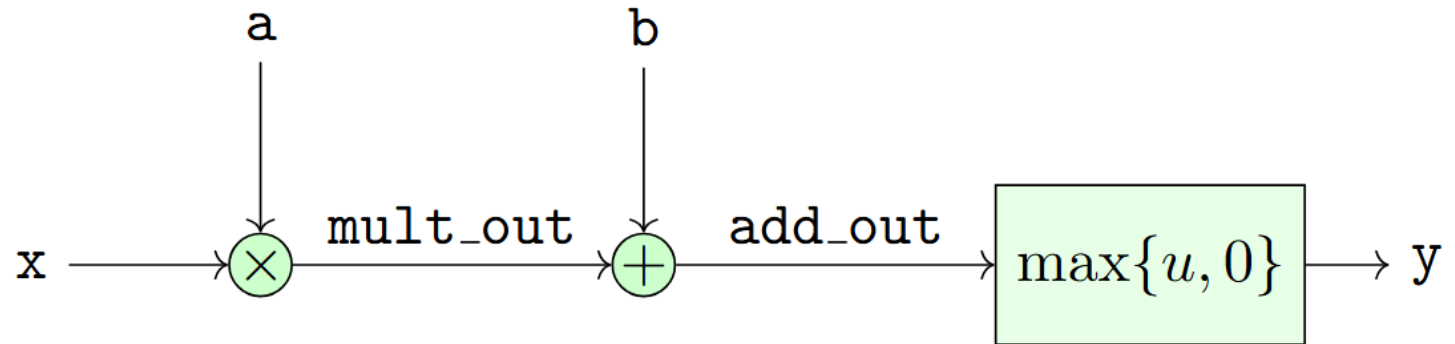
# Block Diagram

- ❑ Function of a module typically represented by a **block diagram**
- ❑ Graphical representation of a potential implementation
- ❑ Typically, diagram is at high-level
  - Adders, multipliers not low-level details components like gates



# Outline

---

☐ Combinational Logic


 ☐ Timing Diagrams for Combinational Logic

☐ Registers, Clocks and Sequential Logic

☐ Simulating and Synthesizing Simple Modules in Vivado
 
# Timing Diagrams

- Graphical representation of the signals in the circuit over time
- Key to analyzing circuits
- Demonstrates:
  - Sequence of operations
  - Latency in each step
  - Critical paths




# Binary Signals

□ Signal: Any time-varying quantity

□ Digital Binary Signals:

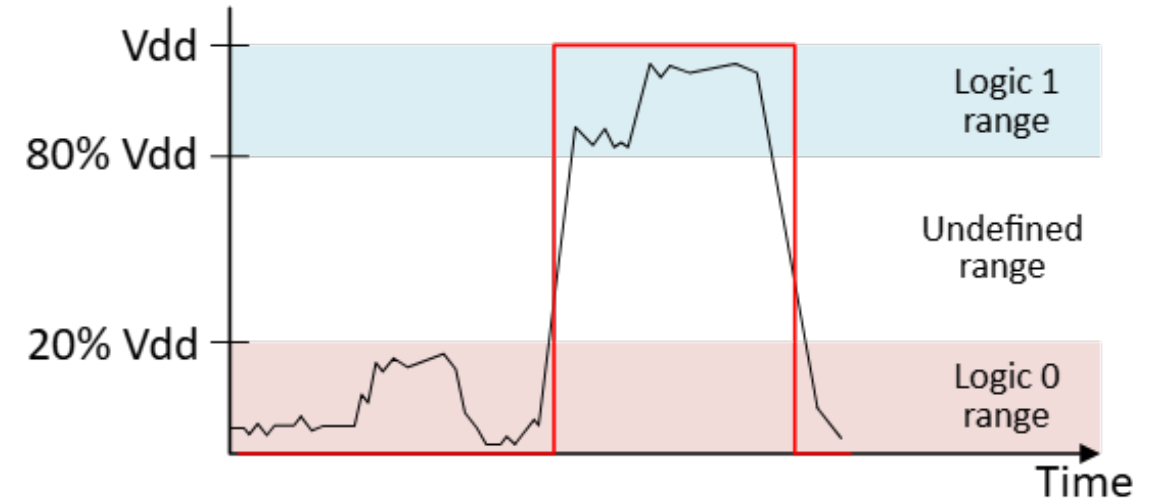
- Two logical values: 0 or 1
- Physically: Typically, a continuous voltage
- Logical value by thresholding




□ Other signals (e.g. integer, floats) built from binary signals
 
# Undefined Logic Value: 'X'

- ❑ Signals take time to transition
  - They are outputs of physical circuits
  - Gates, computational units, ...
- ❑ Creates an **undefined** period
  - Also called indeterminate, unknown, ...
- ❑ Usually denoted as X
- ❑ So binary logic signals have three values:
  - 0, 1 and X
  - Will discuss a fourth value Z later



# Undefined Regions Illustrated

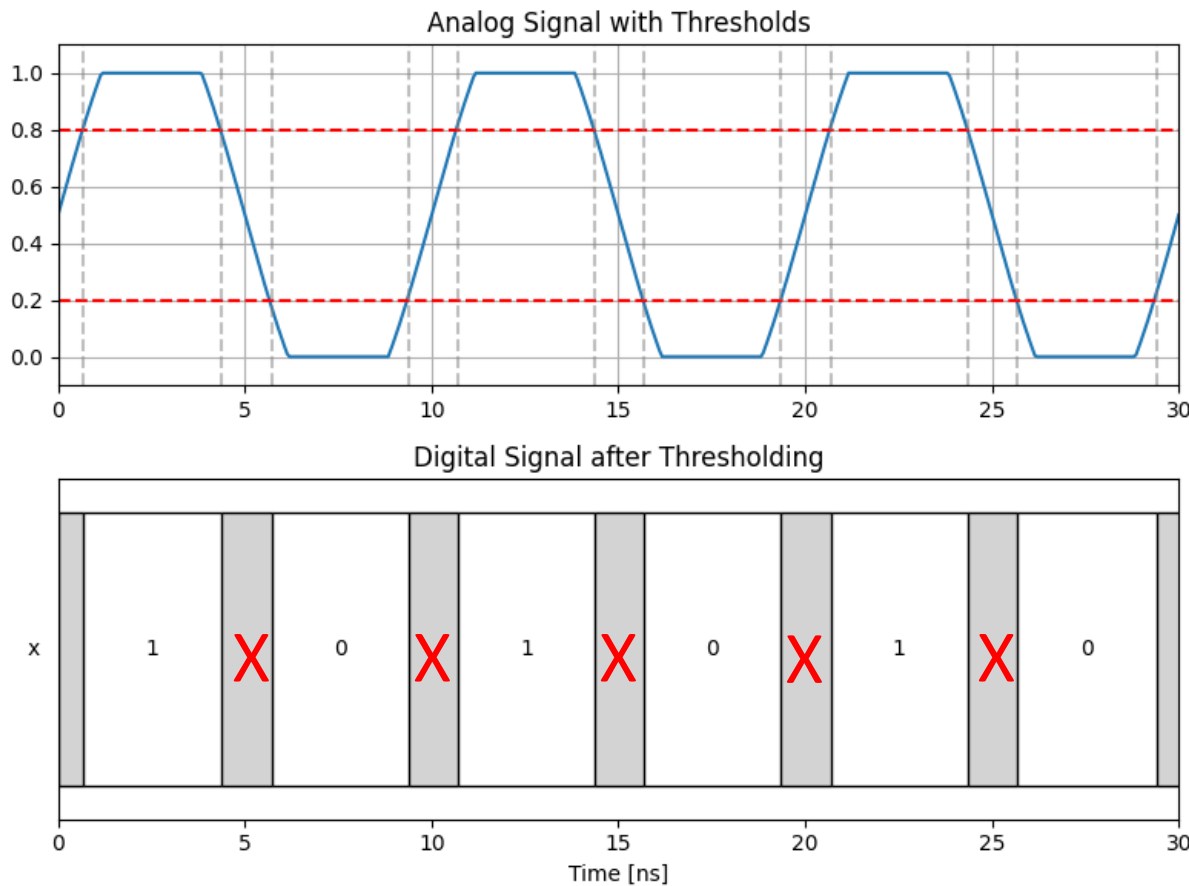

## □ Analog physical signal

- Typically, a voltage
- Continuous valued
- Has finite transition periods

## □ Digital logic signal

- Three values 0, 1 and X
- X value shown in gray

# Value-Change Points

□ In digital logic, signals are often described by their change points

**Definition:** A signal  $x(t)$  has **value-change points**  $\{(t_i, x_i), i = 0, \dots, n - 1\}$  if:

$$x(t) = \begin{cases} X & t < t_0 \\ x_i & t_i \leq t < t_{i+1}, \quad i = 0, \dots, n - 2 \\ x_{n-1} & t \geq t_{n-1} \end{cases}$$

- Value change points also called **valued change events**, **transitions**, ...




# Timing Diagram

- **Timing diagram:** A plot of signals over time showing with value-change points
- Example with two signals:
- VC points for  $x$  :  $\{(3,5), (20,17), (40,8)\}$
- VC points for  $y$  :  $\{(12,3), (25,12), (35,0)\}$
- In this plot, times are in ns



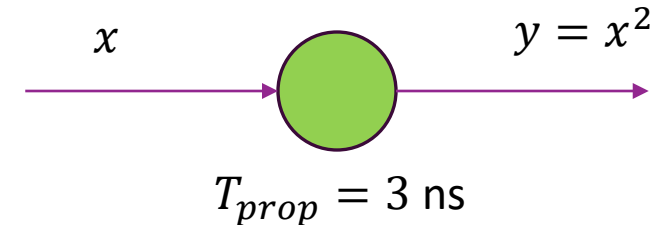
# Propagation Delays

- ❑ Each circuit element incurs a **propagation delay**
  - Time for the output to settle after the input changes
- ❑ On transition of input
  - Output is initially unknown 'X'
  - We cannot assume the value is stable during transition
  - After propagation delay, output settles at value



- ❑ Example:

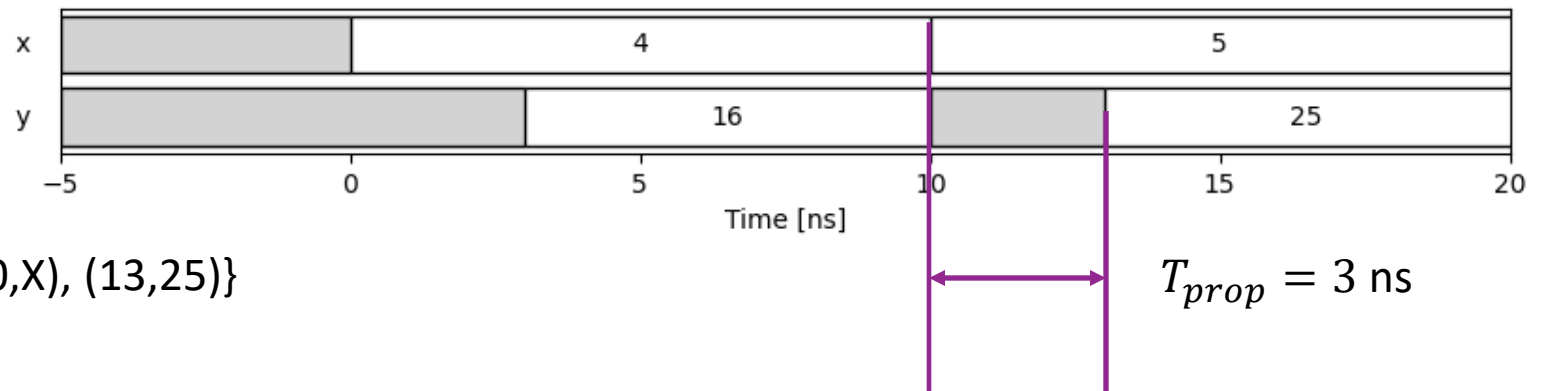- $y = x^2$
- $x$  has VC points  $\{(0,4), (10,5)\}$
- Prop delay is 3 ns
- $y$  has VC points  $\{(0,X), (3,16), (10,X), (13,25)\}$



# Propagation Delays of a Series

□ Our example: Three propagation delays

- Multiplier
- Adder
- Max operator


□ Propagation delays will add

□ Called the **total propagation delay**


- Or **total path delay**

□ Key property: When input  $x$  changes

 
- All downstream values initially go to X




# Example Total Propagation Delay

 

Hardware block	Example Value
Multiplier	$T_{mult} = 3$ ns
Adder	$T_{add} = 1.5$ ns
Max operator	$T_{max} = 1$ ns
Total	$T_{tot} = 5.5$ ns

 

# Example Timing Over Multiple Inputs

 

# Typical Propagation Delays: Low-End FPGA

Hardware block	FPGA resource	Typical range
32-bit adder	LUT + dedicated carry chain	1.5–3.0 ns
16-bit multiplier	DSP48E1 block	2.5–5.0 ns
16-bit comparator	LUT logic + carry chain	1.0–2.0 ns

- ❑ Rough delays for a low-end FPGA (e.g., Pynq Z2)
- ❑ We will explain the FPGA resources more in later units
- ❑ Routing delays not included
  - May be large for more complex designs

# Typical Propagation Delays: ASIC


---

Hardware block	Typical structure	Typical range
32-bit adder	Kogge-Stone / Brent-Kung / hybrid	150-450 ps
16-bit multiplier	Wallace/Dadda tree + final adder	300-700 ps
16-bit comparator	XOR/AND/OR chain with early-out	50-300 ps

- ❑ Rough delays for TSMC 16nm
- ❑ Custom ASICs are much faster than FPGAs
  - Easily 5 to 10x faster
 
# Critical Path

- ❑ Signals may need to propagate over multiple **paths**
- ❑ Each path accumulates different path delay
  - Total propagation time on path
- ❑ **Critical path:**
  - The path with the highest total propagation delay
- ❑ Critical path will determine total delay of module





# Critical Path Example

□ Example: For some functions  $F_1, \dots, F_4$


- $x_1 = F_2(F_1(a))$
- $x_2 = F_3(b)$
- $y = F_4(x_1, x_2)$

□ **Path 1** ( $F_1 \rightarrow F_2 \rightarrow F_4$ ):

- Delay =  $3 + 2 + 2.5 = 7.5$  ns
- Longest = **Critical path**

□ **Path 2** ( $F_3 + F_4$ ):

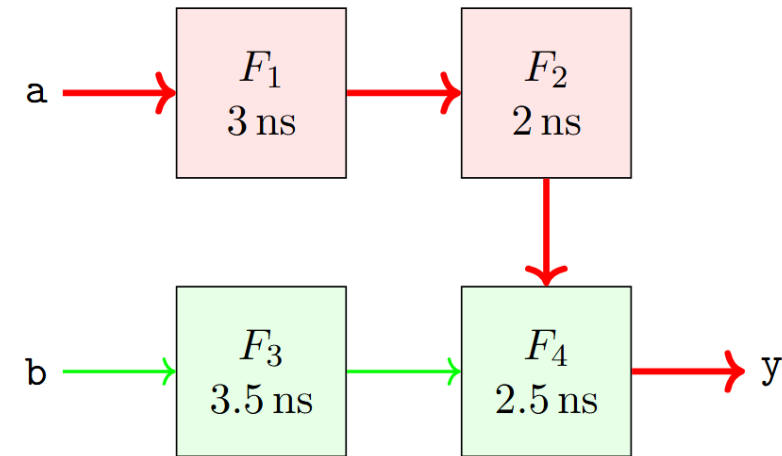- Delay =  $3.5 + 2.5 = 6$  ns
- Shorter = **Non-critical**




# Delay Depends on Implementation

- Example: Consider  $y = a + b + c + d$
- Suppose each add takes  $D$  seconds
- Synthesis tools try to find low delay implementations


Serial implementation

Prop delay =  $3D$

 


Parallel

Prop delay =  $2D$

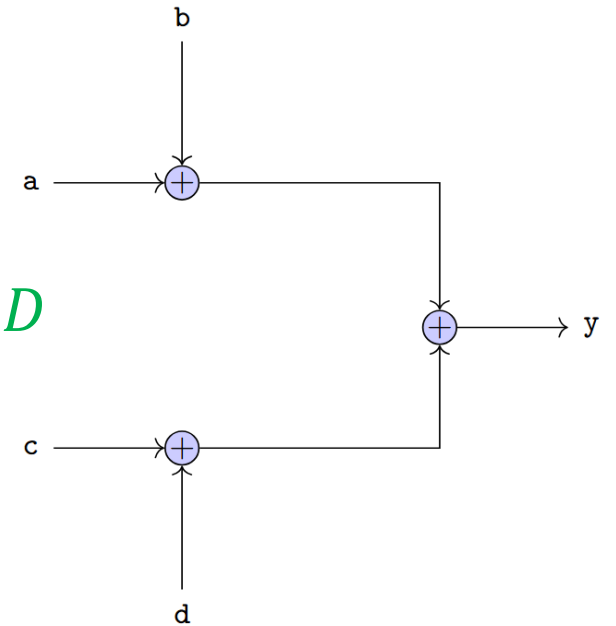


# Outline

---

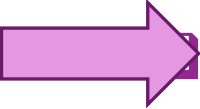- ❑ Combinational Logic
- ❑ Timing Diagrams for Combinational Logic
-  Registers, Clocks and Sequential Logic
- ❑ Simulating and Synthesizing Simple Modules in Vivado
 
# Limitations of Combinational Logic

- ❑ No memory — cannot store past values
- ❑ Output changes immediately with input changes (no control over timing)
- ❑ Long combinational paths lead to large propagation delays
- ❑ Hard to build large systems without controlled timing boundaries
- ❑ Glitches and hazards can propagate freely
- ❑ No notion of “steps” or “cycles” — everything is continuous



# Synchronous (Sequential) Logic


---

- ❑ Introduces **state** via **flip-flops** or **registers**
- ❑ Breaks long logic into **clocked stages**, improving performance
- ❑ Provides **predictable timing** — changes only occur on clock edges
- ❑ Makes large systems modular and easier to reason about
- ❑ Eliminates most hazards/glitches from propagating across stages
- ❑ Enables pipelining, finite-state machines, and sequential algorithms
- ❑ Allows clean interfaces between modules (valid/ready, handshakes, etc.)

Synchronous logic is the dominant paradigm for design

 
# Clock Signal

- ❑ **Clock:** An alternating binary signal
  - Visualized as a square wave
- ❑ Each period is called a **clock cycle**
  - Typically, between two **rising edges**
- ❑ **Parameters:**
  - Clock **period**  $T$
  - **Frequency**  $f = \frac{1}{T}$
- ❑ **Typical parameters:**
  - FPGA logic: 100 to 500 MHz
  - ASIC: 500 MHz to 1 GHz




 
# Synchronous Logic

- ❑ **Key idea:** Save system state on each rising edge
- ❑ Save state in a storage element
  - This unit we will use **registers** (next slide)
- ❑ Brings system to a known state in each cycle
- ❑ Computation can be performed in known steps


  
# Register



- ❑ Basic storage element in synchronous logic
- ❑ On each rising edge of clk:
  - Assigns xreg to x
- ❑ Value of xreg is maintained even if x changes
- ❑ Example below: Input is “sampled” at rising edges
  - Unknown periods not propagated




  
# Register

- ❑ Samples input at each rising edge
- ❑ Input may have X values
  - Not propagated assuming input is valid on positive edges



# Making the Module Synchronous

---

❑ Making module synchronous is easy

❑ First add two inputs to ports

- Clock signal
- Reset on negative edge

```
module relu_lin (  
    input logic clk,   
    input logic rst_n,   
    input logic int x,   
    input logic int a,   
    input logic int b,   
    output logic int y  
);
```

← Clock

← Reset

# System Verilog Main Body

❑ Synchronous logic has two parts

❑ `always_ff`:

- Assigns register outputs
- All operations are in parallel (non-blocking)
- Our example: Saves inputs to registers

❑ `always_comb`:

- Assigns signals via combinational logic
- Operations are sequential (blocking)
- Our example: Computes output from registered inputs


```
int x_reg, a_reg, b_reg;

always_ff @(posedge clk or negedge rst_n) begin
    if (!rst_n) begin
        x_reg <= 0;
        a_reg <= 0;
        b_reg <= 0;
    end else begin
        x_reg <= x;
        a_reg <= a;
        b_reg <= b;
    end
end


always_comb begin
    logic int mult_out, add_out;
    mult_out = x_reg * a_reg;
    add_out = mult_out + b_reg;
    y = (add_out > 0) ? add_out : 0;
end
endmodule
```
 
# Synchronous Block Diagram

- Inputs are registered
- Output is combinational from input



# Synchronous Timing Diagram

 


# Maximum Clock Frequency


- ❑ Consider combinational path
  - xreg, areg, breg → y
- ❑ This path must complete within one clock cycle
- ❑ Otherwise, next input to next stage not correctly sampled

To meet timing:  $T_{clk} > T_{crit}$

 - $T_{crit}$  = delay of critical path,  $T_{clk}$  = clock period
- ❑  $T_{clk} > T_{crit}$  : System **meets timing**
- ❑  $T_{clk} < T_{crit}$  : System **fails timing / timing violation**



# ReLU+Linear Example

 


$$T_{crit} = 5.5 \text{ ns}$$


$$T_{clk} = 10 \text{ ns}$$

Meets timing:  
 $T_{clk} > T_{crit}$

Hardware block	Example Value
Multiplier	$T_{mult} = 3 \text{ ns}$
Adder	$T_{add} = 1.5 \text{ ns}$
Max operator	$T_{max} = 1 \text{ ns}$
Total =critical path	$T_{crit} = 5.5 \text{ ns}$

 


# Max Clock Frequency Example

 

□ Max clock frequency in our example:

 
- $\text{Min } T_{clk} = T_{crit} = 5.5 \text{ ns}$
- $\text{Max clock frequency} = \frac{1}{5.5} \cong 180 \text{ MHz}$




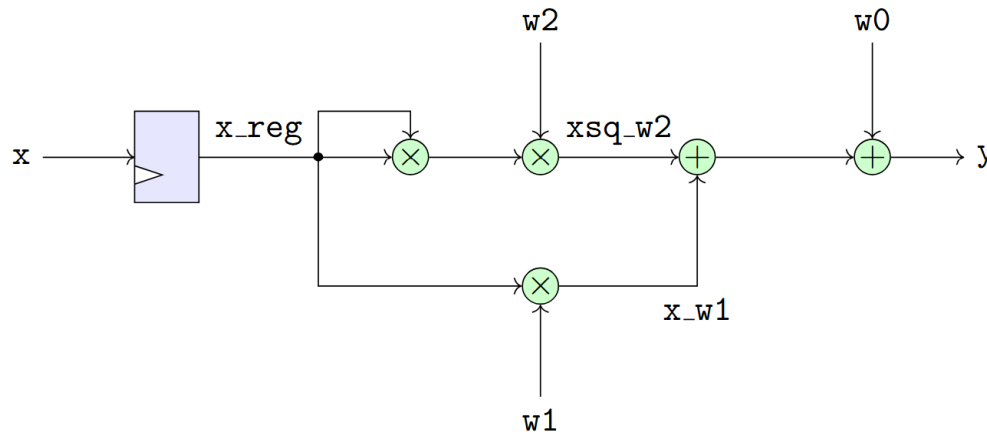
# A More Complex Example


- ❑ Consider a quadratic function:  $y = w_2x^2 + w_1x + w_0$
- ❑ For simplicity, assume  $w_0, w_1, w_2$  are fixed parameters
- ❑ Single cycle implementation to the right



```
module quad_func #(
    parameter int w2 = 0,
    parameter int w1 = 0,
    parameter int w0 = 0
) (
    input logic clk,
    input logic int x,
    output logic int y
);
    int xreg;
    always_ff @(posedge clk) begin
        xreg <= x;
    end
    always_comb begin
        logic int xsq, xsq_w2, x_w1;
        xsq = xreg * xreg;
        xsq_w2 = w2 * xsq;
        x_w1 = w1 * xreg;
        y = xsq_w2 + x_w1 + w0;
    end
end
```

# Finding the Critical Path

Hardware block	Example Value
Register	$T_{reg} = 1 \text{ ns}$
Multiplier	$T_{mult} = 4 \text{ ns}$
Adder	$T_{add} = 1.5 \text{ ns}$
Path 1	$1+4+4+1.5+1.5 = 12$
Path 2	$1+4+1.5+1.5=8$

 

❑ Consider implementation with times in table

❑ Two paths:

❑ Path 1:  $x, x\_reg, xsq\_w2, y$   
◦ 1 register, 2 mults, 2 adders = 12 ns

❑ Path 2:  $x, x\_reg, x\_w1, y$   
◦ 1 register, 1 mult, 2 adders = 8 ns

❑ Path 1 is critical

❑ Max clock frequency =  $\frac{1}{12 \text{ ns}} = 83 \text{ MHz}$


❑ Would **fail timing** at 100 MHz

# A Two Cycle Design

❑ We can improve throughput by breaking computation over two cycles

❑ Register two intermediate terms:

 - $xsq = xreg * xreg$
- $lin\_term = w1 * xreg + w0$



```
int xreg;
always_ff @(posedge clk) begin
    xsq <= xreg * xreg;
    lin_term <= w1 * xreg + w0;
    xreg <= x;
end
always_comb begin
    y = w2*xsq + lin_term;
end
```

# Three Stages

❑ Designs is processed in three stages = 2 cycles

❑ Stage 0

- Register input  $x$  to `xreg`

❑ Stage 1: Compute and register:

- $xsq = xreg * xreg$
- $lin\_term = w1 * xreg + w0$


❑ Stage 2: Compute output

- $y = w2 * xsq + lin\_term$

```
int xreg;
always_ff @(posedge clk) begin
    xsq <= xreg * xreg;
    lin_term <= w1 * xreg + w0;
    xreg <= x;
end
always_comb begin
    y = w2*xsq + lin_term;
end
```

# Critical Path with Three Stages

Hardware block	Example Value
Register	$T_{reg} = 1 \text{ ns}$
Multiplier	$T_{mult} = 4 \text{ ns}$
Adder	$T_{add} = 1.5 \text{ ns}$
Path 1	$1+4=5$
Path 2	$1+4+1.5=6.5$
Path 3	$1+4+1.5=6.5$

 

❑ Measure paths from register to register

❑ Path 1:  $x, x\_reg, xsq$  input

- 1 register, 1 mult = 5 ns

❑ Path 2:  $x, x\_reg, w1\_x, lin\_x$  input

- 1 register, 1 mult, 1 add = 6.5 ns


❑ Path 3:  $xsq\_reg, lin\_x, w2\_xsq, y$

- 1 register, 1 mult, 1 add = 6.5 ns

❑ Critical path delay = 6.5 ns

❑ Max freq =  $\frac{1}{6.5} \approx 153 \text{ MHz}$

# Two Cycle Timing Diagram

 

Example with

$w = [4, -7, 5]$

$x$  inputs 10, -4, 8

# Latency, Throughput and Pipelining

□ Suppose that we run at our design at 100 MHz clock

□ Latency:


- Suppose input is valid on rising edge of clock  $n$
- Then output is valid before rising edge of clock  $n + 2$
- Latency = 2 clock cycles = 20 ns

□ Throughput:

- Circuit can take a new input each cycle
- Throughput = 1 input / cycle = 100 MHz

□ Process is called a pipeline

 - Circuit is processing multiple inputs at the same time



# Performance Comparison


	Single Cycle Design	Two Cycle Design
Critical path	12 ns	6.5 ns
Max clock frequency	$\approx 80$ MHz	$\approx 150$ MHz
Max throughput	80 MHz	150 MHz
Latency	1 cycle = 12 ns	2 cycles = 13 ns

*Pipelining benefit:  
For small increase in latency, we dramatically improve throughput*



# Outline

---

- ❑ Combinational Logic
- ❑ Timing Diagrams for Combinational Logic
- ❑ Registers, Clocks and Sequential Logic
-  Simulating and Synthesizing Simple Modules in Vivado