

Introduction to Hardware Design

Basic Digital Logic: Figures and Code Snippets

Profs. Sundeep Rangan, Siddharth Garg

0.1 Combinational Example: ReLU with a linear input

We consider implementing the ReLU function:

$$y = \max\{ax + b, 0\}$$

where x , a , and b are integer inputs. This function arises commonly in machine learning. We first consider a purely combinational implementation of this function. A possible SystemVerilog implementation is as follows:

```
module relu_lin (  
  input logic int x,  
  input logic int a,  
  input logic int b,  
  output logic int y  
);  
  always_comb begin  
    logic int mult_out, add_out;  
    mult_out = x * a;  
    add_out = mult_out + b;  
    y = (add_out > 0) ? add_out : 0;  
  end  
endmodule
```

When this module is synthesized, a potential block diagram is as shown in Figure ??.

0.2 Adder

Implementation of $y = a + b + c + d$. First, we show a serial implementation:

Next, we show a parallel implementation:

$$z_1 = a + b$$

$$z_2 = c + d$$

$$y = z_1 + z_2$$

 


Figure 1: Fully combinational block diagram for ReLU with a linear input.

 


Figure 2: Serial implementation of an adder.

 


Figure 3: Critical path of a circuit. Critical path highlighted in red.

 


Figure 4: Parallel implementation of an adder.

 


Figure 5: Basic register block diagram.

 


Figure 6: Synchronous version of ReLU with a linear input.

0.3 Register

Draw a basic register.

0.4 Sequential ReLU with a linear input

The sequential implementation of the ReLU with a linear input is as follows:

```

module relu_lin (
    input logic clk,
    input logic rst_n,
    input logic int x,
    input logic int a,
    input logic int b,
    output logic int y
);
    int x_reg, a_reg, b_reg;

    always_ff @(posedge clk or negedge rst_n) begin
        if (!rst_n) begin
            x_reg <= 0;
            a_reg <= 0;
            b_reg <= 0;
        end else begin
            x_reg <= x;
            a_reg <= a;
            b_reg <= b;
        end
    end

    always_comb begin
        logic int mult_out, add_out;
        mult_out = x_reg * a_reg;
        add_out = mult_out + b_reg;
        y = (add_out > 0) ? add_out : 0;
    end
endmodule

```

 


Figure 7: Single cycle implementation of a quadratic function.

0.5 Quadratic Function with a Single Cycle

We wish to implement the function:

$$y = w_2x^2 + w_1x + w_0$$

A single cycle implementation is as follows treating w_i as fixed parameters is:

```

module quad_func #(
    parameter int w2 = 0,
    parameter int w1 = 0,
    parameter int w0 = 0
) (
    input logic clk,
    input logic int x,
    output logic int y
);
    int xreg;
    always_ff @(posedge clk) begin
        xreg <= x;
    end
    always_comb begin
        logic int xsq, xsq_w2, x_w1;
        xsq = xreg * xreg;
        xsq_w2 = w2 * xsq;
        x_w1 = w1 * xreg;
        y = xsq_w2 + x_w1 + w0;
    end
end
  
```

The block diagram is as shown in Figure ??.

0.6 Quadratic Function with a Multi-Cycle Pipeline

A single cycle implementation is as follows treating w_i as fixed parameters is:

```

module quad_func #(
    parameter int w2 = 0,
    parameter int w1 = 0,
    parameter int w0 = 0
) (
    input logic clk,
    input logic int x,
    output logic int y
);
  
```

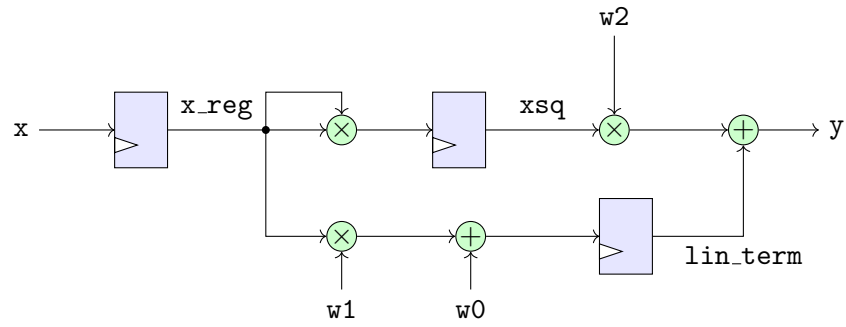


Figure 8: Two cycle implementation of a quadratic function.

```

int xreg;
always_ff @(posedge clk) begin
    xsq <= xreg * xreg;
    lin_term <= w1 * xreg + w0;
    xreg <= x;
end
always_comb begin
    y = w2*xsq + lin_term;
end
endmodule

```